
hardwear.io

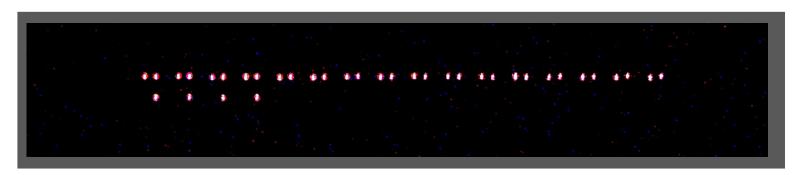
Extracting programmable logic with photons



John McMaster McMaster Consulting

Infrared (IR) emissions

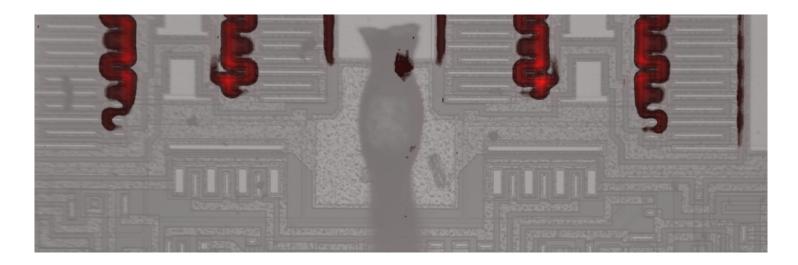- Emitted during electron recombination
- Emitted at the bandgap of silicon: ~1.14 eV => 1088 nm
- Can correlate emissions to circuit activity



Previous talk: use a sensitive \$500 CMOS camera

- Back illuminated CMOS
- Remove IR block filter, install IR pass filter




E3ISPM20000KPA




Previous talk: RE bipolar logic based on emissions


2 input NAND gate

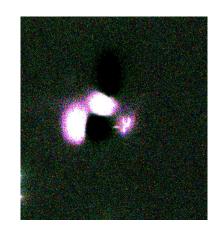


I1: L, I2: L O: H

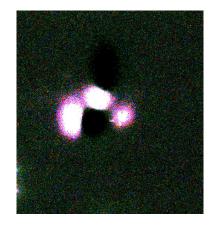

I1: H, I2: L O: H

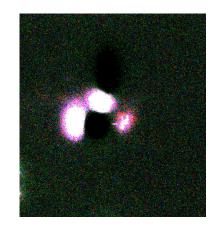

I1: L, I2: H O: H

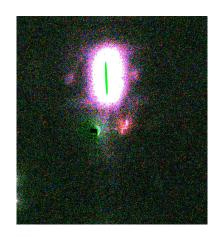

I1: H, I2: H O: L

This is all good but...


- Research / theoretical on simple devices
- How can we apply this in the real world?
- Get creative: what can we do outside of cryptography?

TrackStar documentation project

- TrackStar 128 allows running Apple][programs on a PC
- Crazy! How does it work?
- Problem: logic devices are protected. What next?




PAL16R8 (DM3428)

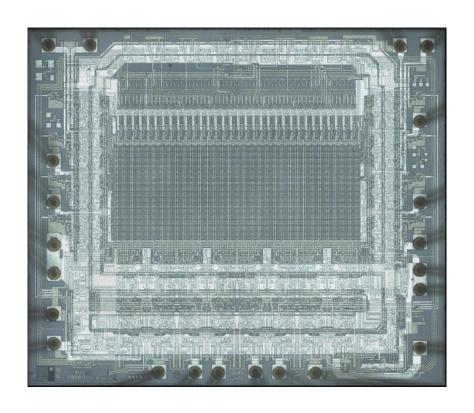

Brute forcing PAL devices

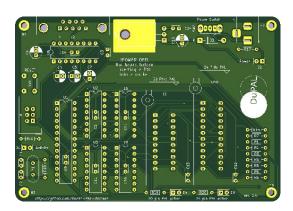
- PAL's are relatively simple. Why not just apply all the input permutations?
- Existing projects: readpal, DuPAL, etc
- Played with pal866 (open-tl866) to avoid custom hardware
- May produce equivalent firmware, not the original






Can it be treated like a mask ROM?

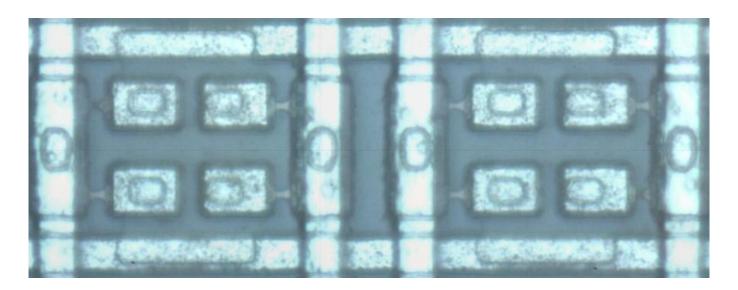
- Yes! Fuses are visible under microscope
- Use existing rompar etc workflow
- But what is the memory layout?



Emissions to the rescue

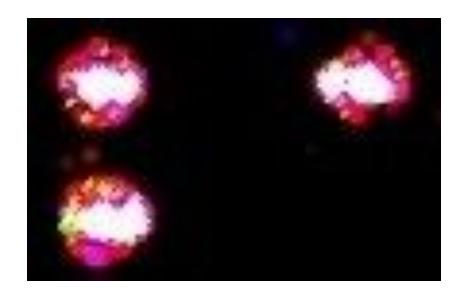- Blowing fuse => massive light emission
- Blow one fuse at a time to map memory layout



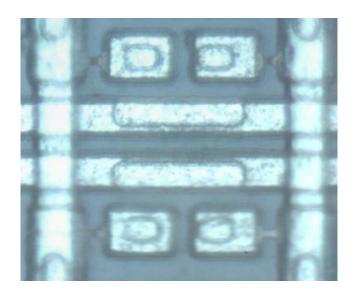


Automation


- AutoHotkey script drives BP Microsystems GUI
- AutoHotkey TCP server takes JSON from Linux Python program
- Camera in time lapse mode
- Python script synchronized to frame saving




Automation

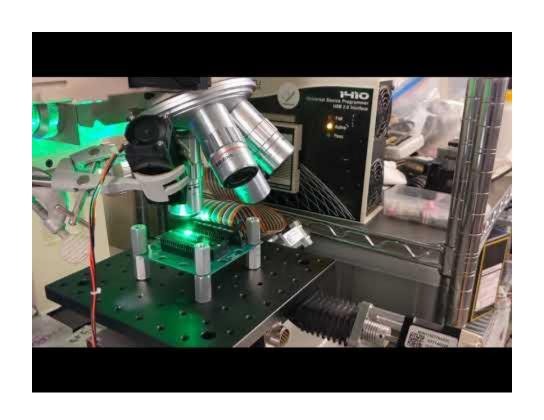

Abracadabra! inter-word layout

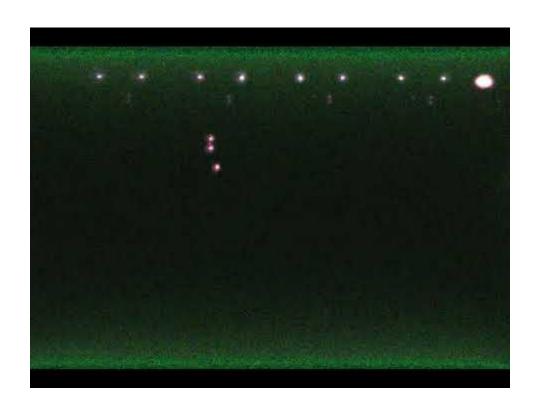


Abracadabra! intra-word layout (word 30)

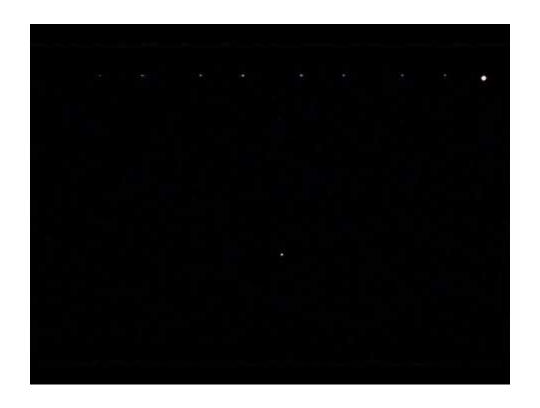

Verification

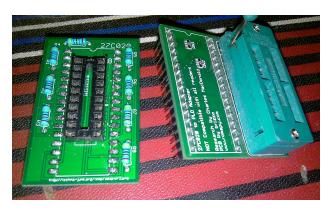- MCU mask ROM => disassemble
- Logic => valid circuits?
- Convert .JED to verilog, compare against test waveforms




https://www.arcade-projects.com/threads/help-me-solve-an-ssv-mystery.12138/

Putting it together

- Collect test vectors from PAL device
- 2. Decap PAL device
- 3. Photograph PAL
- 4. Convert photographs into bit matrix (manually, rompar, etc)
- 5. Convert bit matrix to JED using custom Python program
- 6. Convert JED into Verilog (MAME?)
- 7. Verify test vectors against Verilog
- 8. Pretend it worked
- 9. Do something better


Can we do better?

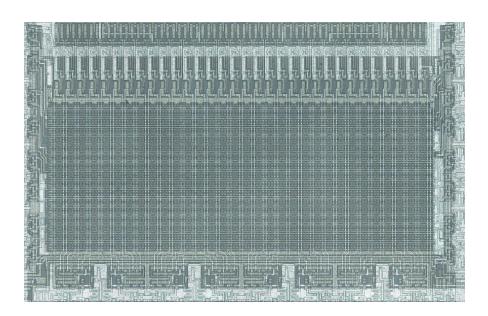- If we can instantly locate a fuse, why not just locate the security fuses (2)?
- Theory: they are related to the extra fuses along the edges



Disappointment

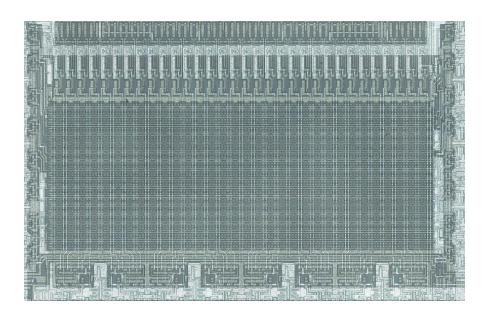- No security fuses visible while burning :(
- Maybe hidden under metal?





Datasheet to the rescue

- 1986_National_Programmable_Logic_Design_Guide.pdf
 - "Note 2: It is recommended that precautions be taken to minimize electrostatic discharge when handling and testing this product. Pins 1 and 11 are connected directly to the security fuses..."
- Let's try again!


Viola!

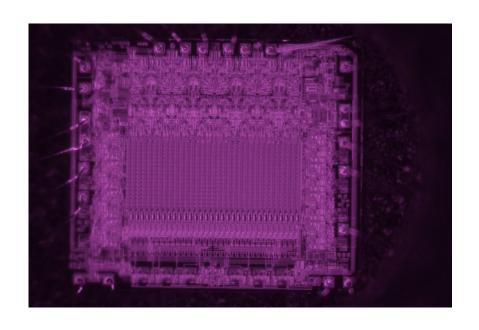Two bright spots indicating security fuses




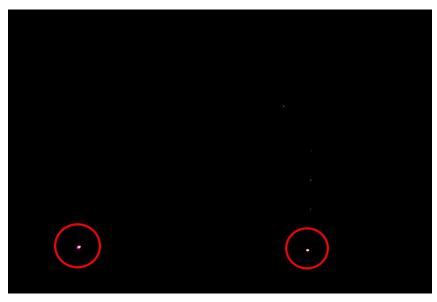

Can we see it burn in real time?

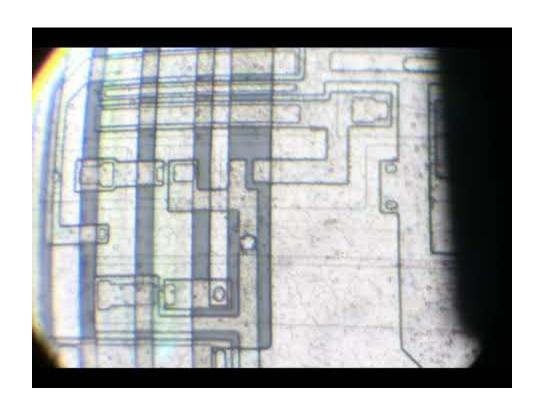

Secured fuse close up

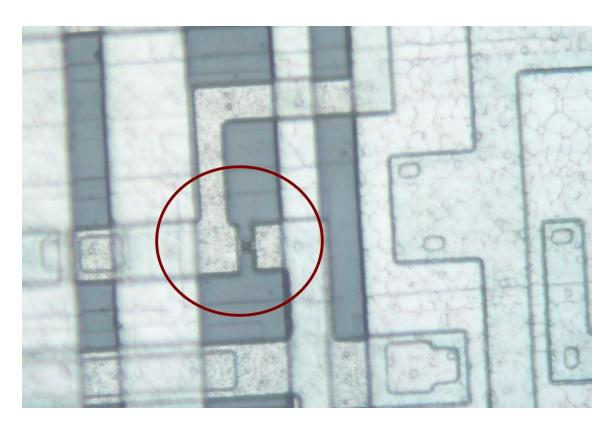

What next?


- Microprobe security fuses to remove protection
- How:
 - 1) Use laser probe station to cut holes in overglass to expose metal
 - 2) Microprobe exposed circuit traces to force logic value


How to probe?


- Take scope traces before / after security to understand logic states
- Ideally constant value (VCC/GND) => don't need to actually bridge fuse
- Old/big logic => not using active probes



Time to put some photons in

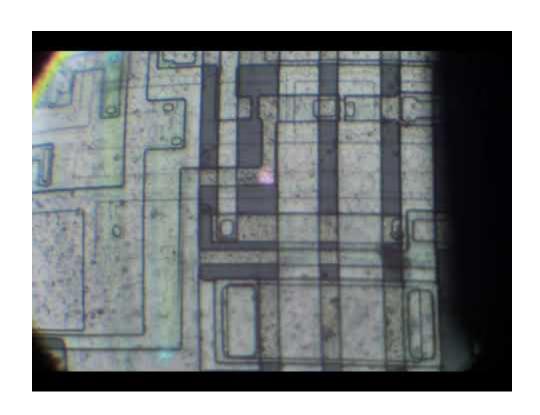


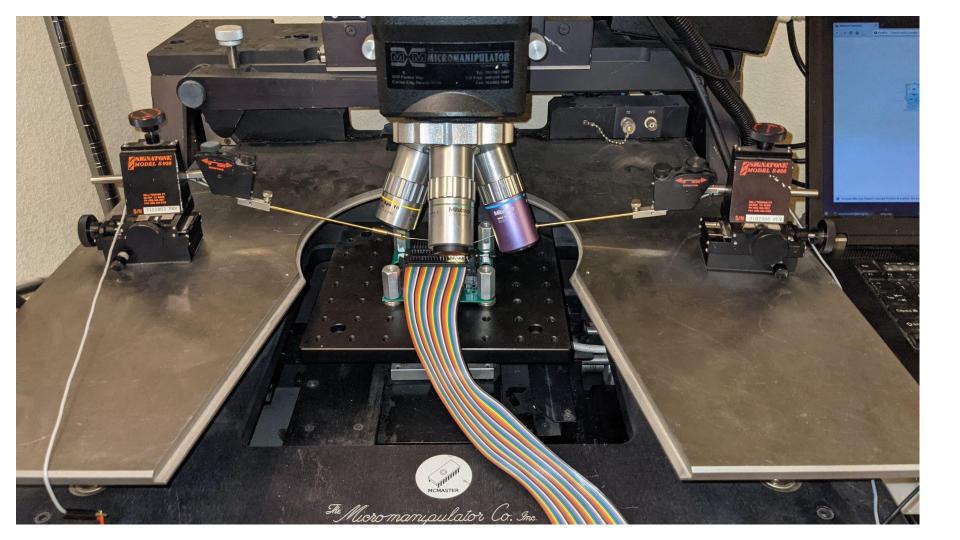

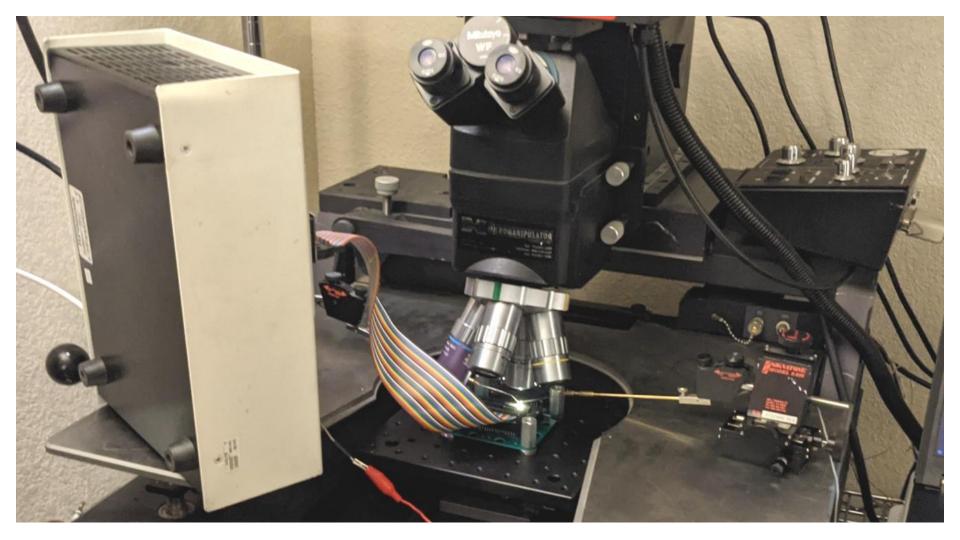


Oopsie daisy...short circuit

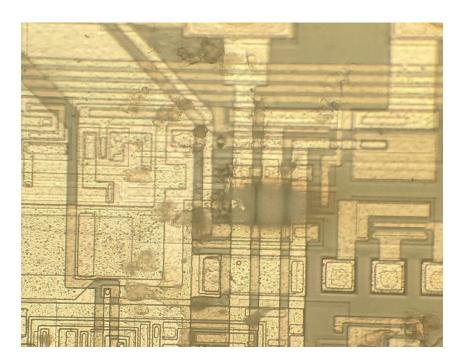• Tungsten probe somehow melted before the IC trace!




Try probing again...

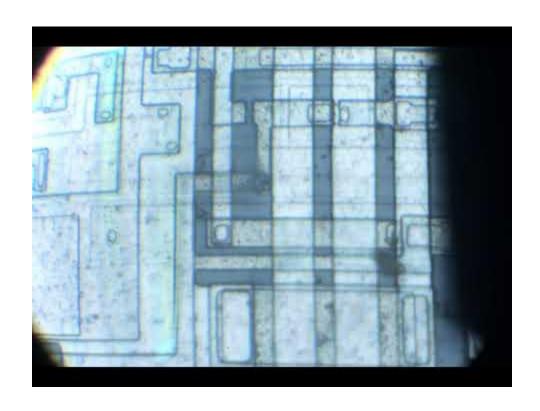


An unexpected result

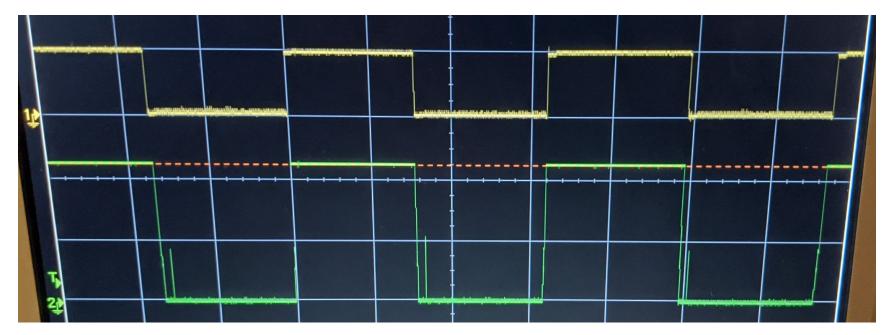- Not constant VL or VH => analog / specialized circuit?
- 5V (inner die) and ~12V (outer die) observed




External power made it sad


Tried both sides

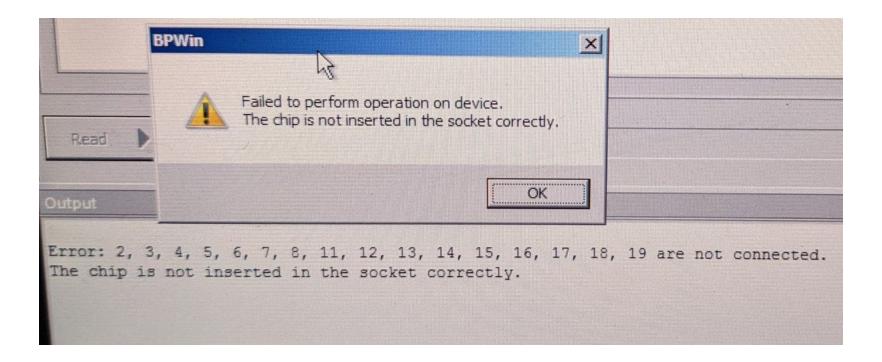

...so just bridge the contacts w/ two microprobes

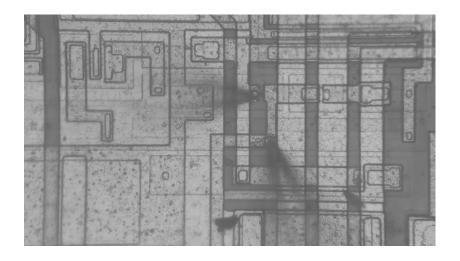- Success! But half of the data => do twice
- PoC here but also worked on Trackstar PAL16R8



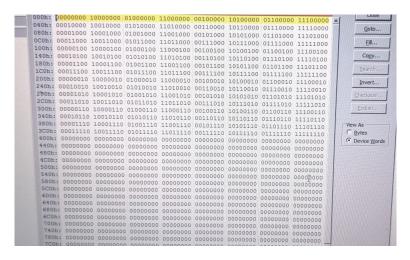

Epilogue (if time)

Need better camera for more modern applications?

- InGaAs cameras! Non-silicon IC
- More sensitive but short exposure time :(
- Neither useful in practice




What else is out there?

- Last time: cooled camera had low noise, but CMOS had best sensitivity
- Could we get a cooled CMOS detector? Yes!
- \$\$\$ but scrapped out of surplus medical device
- Special thanks to Bayley of <u>oneTesla</u> for loaning me this camera!




Improved enclosure

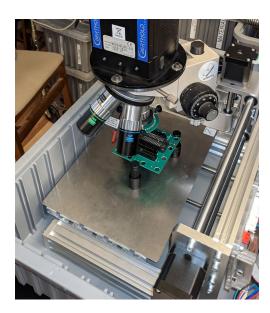
- Mount camera on low cost CNC to manipulate in the dark
- More properly sealed enclosure



EPROM / flash?

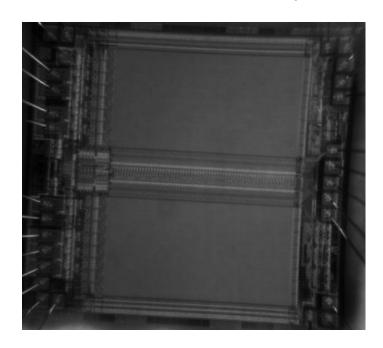- EPROM plausible, flash no
- TODO: EPROM security fuse (ex: 8751, PIC)



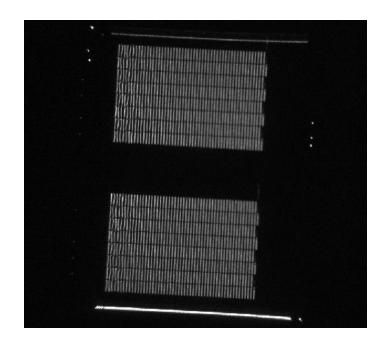

Future work

- Antifuse
- EPROM security fuses
- Bridge w/ silver epoxy?




Special thanks

- Ethan Wright: helping with lab work
- Bayley Wang: cooled Apogee camera
 - https://onetesla.com/
- Brandon Cobb: Trackstar support, partial funding
 - http://www.diskman.com/



Thanks for listening!

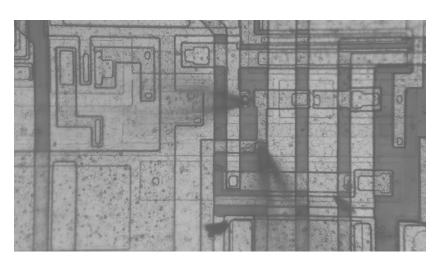- @johndmcmaster
- BP Microsystems AHK: https://github.com/JohnDMcMaster/bpmicro
- pal16 scripts: https://github.com/JohnDMcMaster/icfuzz
- pal866: https://github.com/JohnDMcMaster/pal866



Backup

Summary

- Fuse burning readily visible under microscope
- EPROM was visible in some of my tests
- Flash was not visible in my tests

Demo?

- Questions first?
- Step 1: find fuses
- Step 2: microprobe security

Bit matrix to Verilog workflow

- python3 txt2jed.py capture.txt capture.jed
- jedutil -convert capture.jed capture_mame.bin
- python3 pal16r8_to_verilog.py capture_mame.bin >capture.v

Laser settings

- Green, High-650
- Marker around 2.25 / 2.25

An unexpected result

- Not VL or VH => analog / specialized circuit
- Options:
 - 1) Emulate voltage externally
 - 2) Bridge fuse(s)

	Blank	Secure (outer)	Secure (inner)
Left	1.62V	1.70V	Oops
Right	1.55V	1.47V	0.01V